


MPSL2020

Lab3


Components of lab

- Breadboard
- 4DIP Switch
- 1K Ω Network Resistor *1
- LED *4
- 220 Ω resistor *4

Breadboard

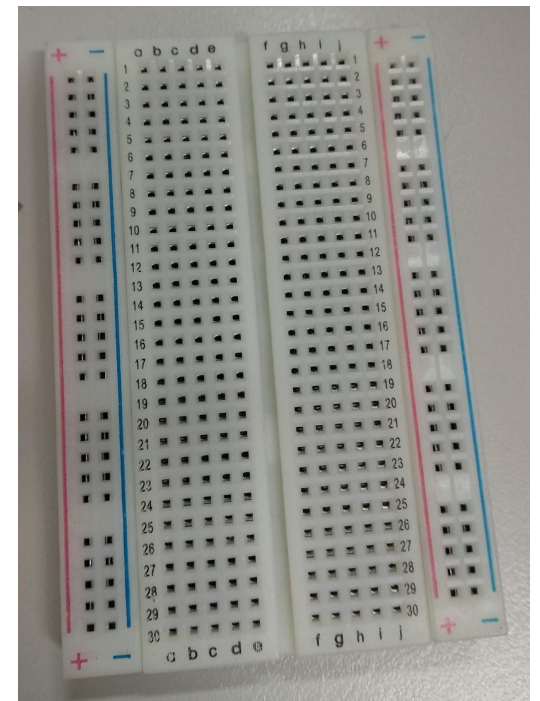

4 DIP Switch

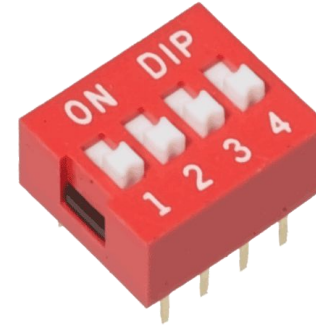

1k Ω Network resistor



LED * 4



220 Ω resistor *4




Breadboard

- Easy to connect electronic components
- Please be careful when plugging and unplugging



vertical
connec
tion

直向相通

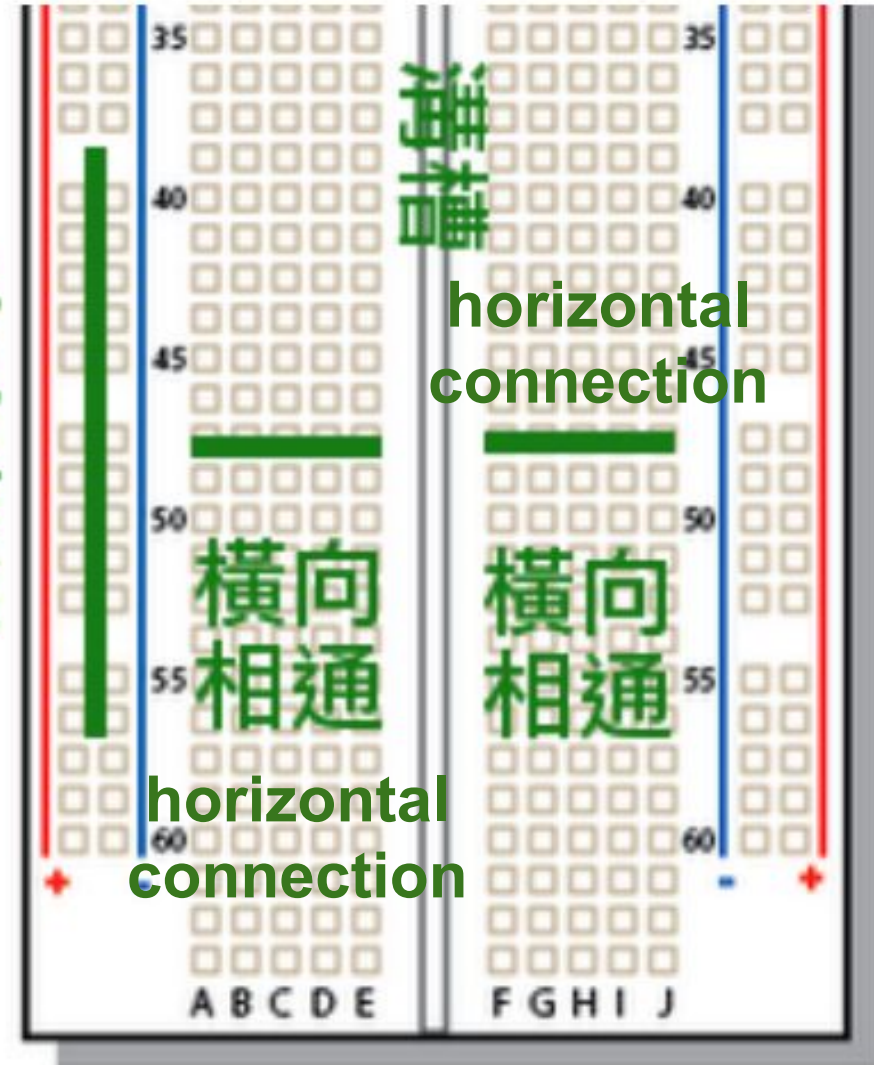

Resistor and LED

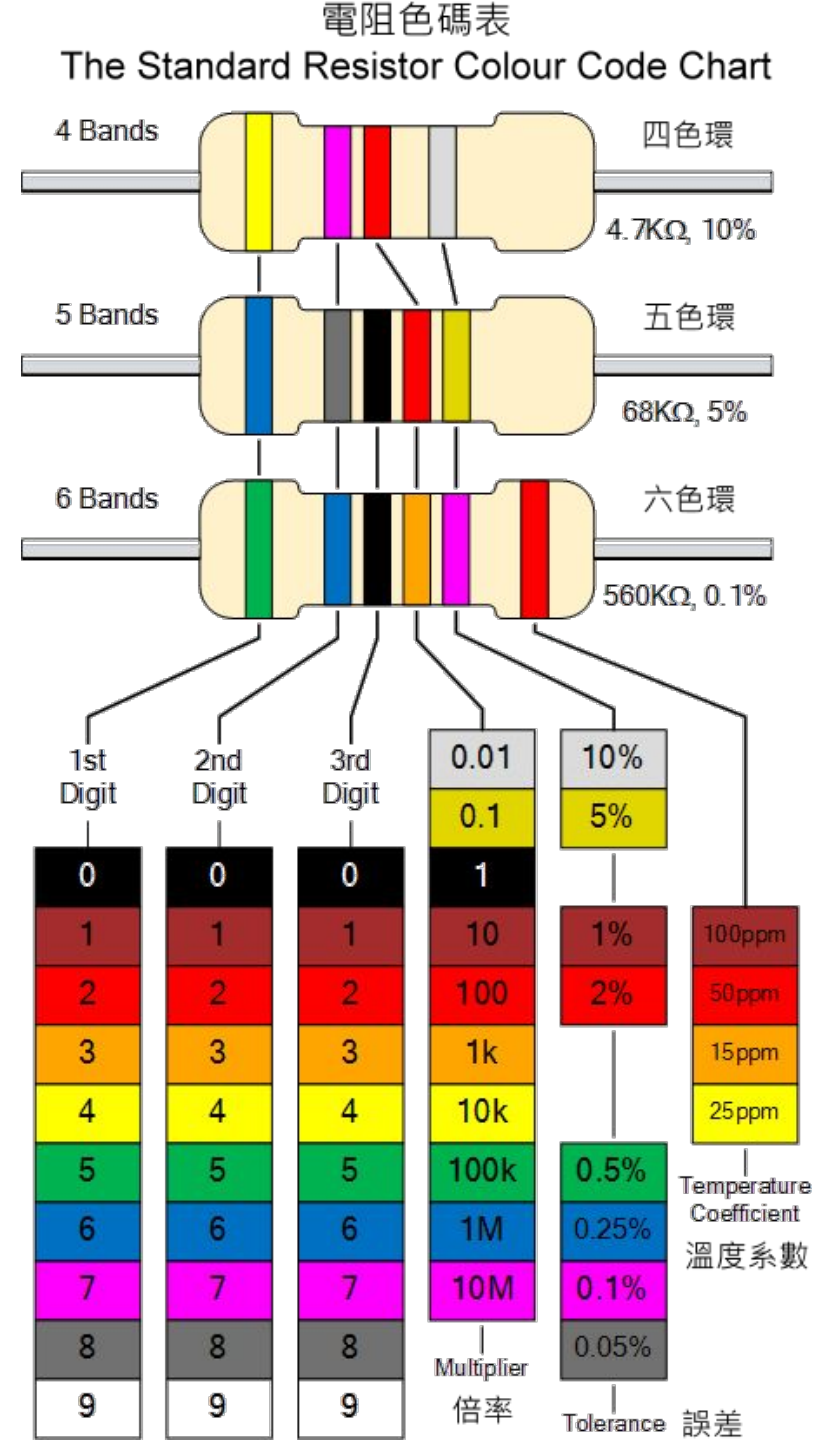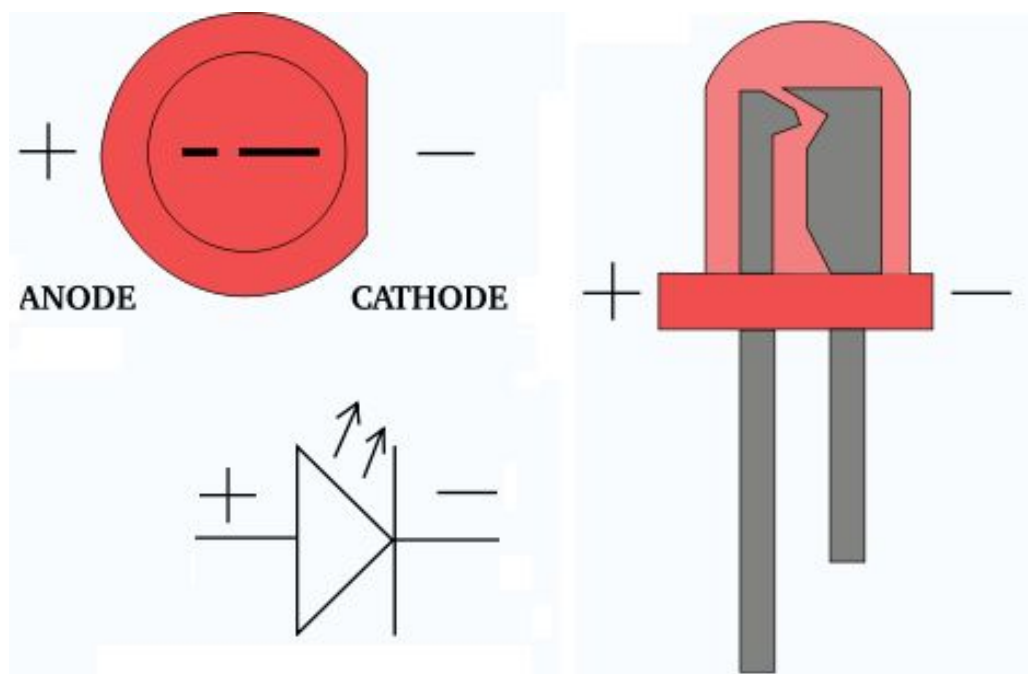- mark resistor value by colour code
- the long pin of LED is positive (+)




Network resistor 排列電阻

- many resistors in it
- mark resistor value by number, e.g : $102=10*10^2 = 1K \Omega$

| network resistor naming | | | |
|--|----------------|---|--|
| circuit type | number of pins | resistor value | difference |
| <ul style="list-style-type: none">• A : all resistors share one pin (leftmost)• B : each resistor has its own independent pin• ... | 4 ~ 14 | three-digital first and second digital are valid number and third digital is number of zero after valid number | <ul style="list-style-type: none">• F : $\pm 1\%$• G : $\pm 2\%$• J : $\pm 5\%$ |

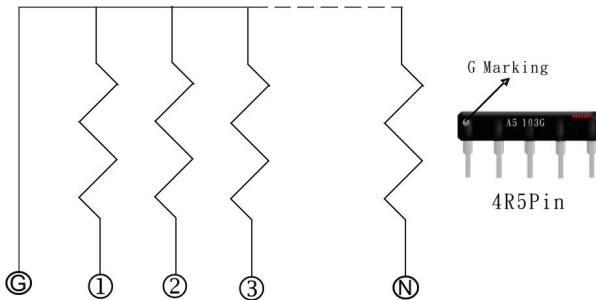直立式排列電阻 A 電路
Network Resistor Circuit - A Type



Our network resistor name is "A 102 J".
The "A" means all resistors share one pin.
102 means $1K \Omega$

Negative logic and Positive logic

- logic can mean to the logical level received by the CPU when a component "action" or "trigger"
- Positive logic or Active High
 - When component actions, CPU receives High level ("1")
- Negative logic or Active Low
 - When component actions, CPU receives Low level ("0")

